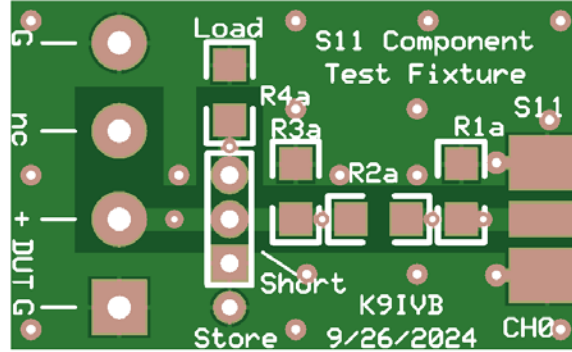


S11 Component Fixture – Shunt Measurements

This fixture was inspired by Rusty, KJ6AMR's NanoVNA 101 Class [copies at <https://bit.ly/KJ6AMR>]. The primary purpose is to make component measurements in the S11 mode with a NanoVNA.



The circuit schematic is very simple and includes an attenuator with a screw terminal block, in addition to a load and short configuration for calibration. The open is just the fixture with nothing connected. The user can connect the fixture to the NanoVNA through a male or female Edge Mount SMA connector. A male SMA allows direct connection to the S11 port.

There are many attenuator configurations that can be used, including none or 0 dB with a 0 Ohm resistor for R2. The most familiar would be a symmetrical 50 Ohm = Z_0 in / out with only two values. The parts list below provides an 8.2 dB configuration. Note the PCB was designed with 1206 pads but 0805 parts will fit and are more reasonably priced in 0.1% values.

8.25 dB Attenuator Symmetrical - 50 Ω = Z_0 in / out

| Ref Des | Description | Mouser Part # |
|---------|---|-------------------|
| R1a,R3a | Thin Film Resistors - SMD 0805 1/8W 113 ohm 0.1% 25ppm | 667-ERA-6AEB1130V |
| R2a | Thin Film Resistors - SMD 0805 1/8W 54.9 ohm 0.1% 25ppm | 667-ERA-6AEB54R9V |

All 50 Ohm Fixtures where DUT R_0 = 50 Ohms

| | | |
|-----------|---|-------------------|
| R4a, R4b, | Thin Film Resistors - SMD 0805 1/8W 100 ohm 0.1% 25ppm | 667-ERA-6AEB101V |
| Or R4a | Thin Film Resistors - SMD 0805 1/8W 49.9 ohm 0.1% 25ppm | 667-ERA-6AEB49R9V |

Note; If you are using a non 50 Ohm R_0 customized attenuator you will need to use off board S-O-L Calibration. If you know the R_0 , then the value of $R4 = R_0$ and on board calibration S-O-L can be used.

Please refer to the short form descriptions in the document "Excerpts from some of Sam Wetterlins' Documents".

<http://www.k9ivb.net/NanoVNA/Excerpts%20from%20some%20of%20Sam%20Wetterlins%20Documents.pdf>

When looking for resistor values for attenuators three web sites provide very easy to use on line calculators.

For two series or parallel resistors to achieve a specific value

<http://mustcalculate.com/electronics/resistorfinder.php?r=50.25&es=E96>

A Matching Pi Attenuator Calculator that handles Unsymmetrical Pi Attenuators and provides data and equations. <https://chemandy.com/calculators/matching-pi-attenuator-calculator.htm>

A useful alternative with multiple configurations. https://k7mem.com/Res_Atenuator.html

K9IVB 10/06/2024